
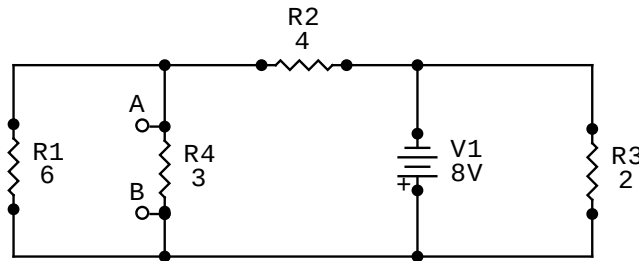


ENPH 334/PHYS 334 – Class Problems, Week 1

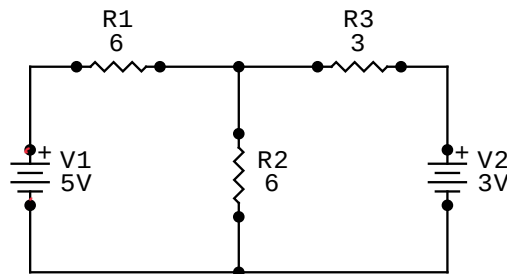1. Find the Thevenin equivalent circuit between points (A,B), with R4 removed.



2. Use Superposition to find the voltage across R2 and the current through R1.



3. [Exercise 6.24] A sinusoidal voltage of 12 V at 500 Hz is applied across a series combination of a 5 k Ω resistor and a 100 nF capacitor. Use a phasor diagram to determine the current through the combination, and the phase angle between this current and the applied voltage.